


Spóla + raunviðnáð
Raðtenging

$$U_Z = \sqrt{U_R^2 + U_L^2}$$

$$Z = \sqrt{R^2 + X_L^2}$$

$$I_Z = \frac{U_Z}{Z}$$

$$\cos \varphi = \frac{U_R}{U_Z}$$

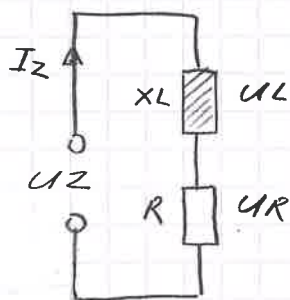


Spóla + raunviðnáð
Hliðtenging

$$I_Z = \sqrt{I_R^2 + I_L^2}$$

$$Z = \frac{U_Z}{I_Z}$$

$$I_R = \frac{U_R}{R} \quad I_L = \frac{U_L}{X_L}$$

$$\cos \varphi = \frac{I_R}{I_Z}$$

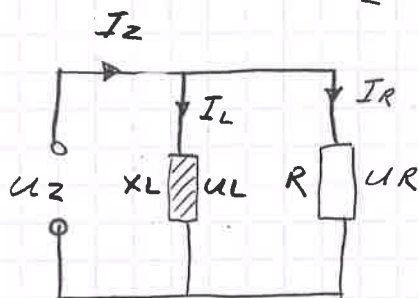


Þéttir + raunviðnáð
Raðtenging

$$Z = \sqrt{R^2 + X_C^2}$$

$$I_Z = \frac{U_Z}{Z}$$

$$U_Z = \sqrt{U_R^2 + U_C^2}$$

$$\cos \varphi = \frac{U_R}{U_Z}$$

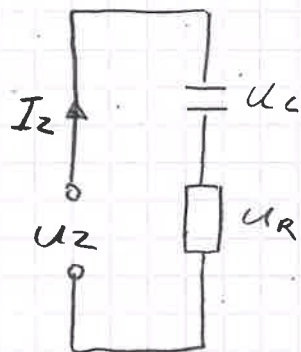


Þéttir - raunviðnáð
Hliðtenging

$$I_Z = \sqrt{I_R^2 + I_C^2}$$

$$Z = \frac{U_Z}{I_Z}$$

$$I_R = \frac{U_R}{R} \quad I_C = \frac{U_C}{X_C}$$

$$\cos \varphi = \frac{I_R}{I_Z}$$

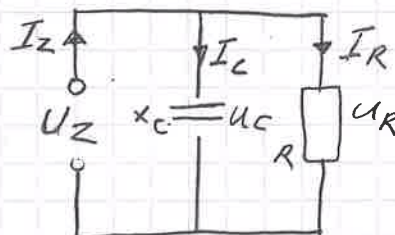

Vidnáðir:

$$X_C = \frac{1}{2 \cdot \pi \cdot f \cdot C}$$

$$X_L = 2 \cdot \pi \cdot f \cdot L$$


X_C = Launviðnáð þéttis
 X_L = Launviðnáð spólu
 R = Raunviðnáð

Eigintíðni:

Eigintíðni er þegar $X_L = X_C$

$$f = \sqrt{\frac{1}{4 \cdot \pi^2 \cdot L \cdot C}}$$

Raunviðnám + spóla + þéttir
Röðtenging.

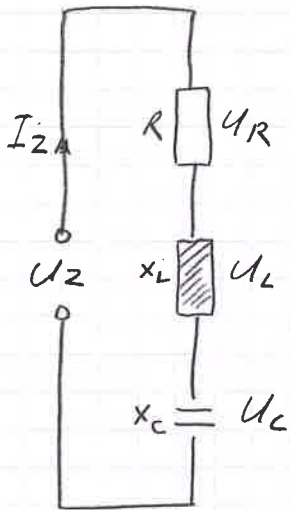

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$


$$U_Z = \sqrt{U_R^2 + (U_L - U_C)^2}$$

$$P = U \cdot I \cdot \cos \varphi$$

$$\cos \varphi = \frac{U_R}{U_Z}$$

Raunviðnám + spóla + þéttir
Hliðtenging.

2.

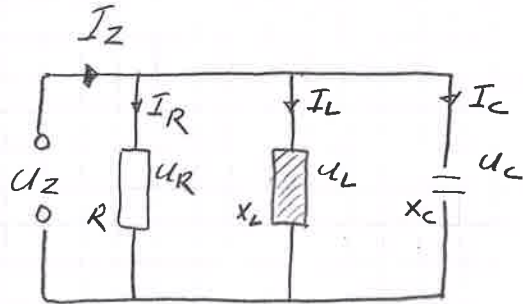


$$I_Z = \sqrt{I_R^2 + (I_C - I_L)^2}$$

$$Z = \frac{U_Z}{I_Z}$$

$$\cos \varphi = \frac{I_R}{I_Z}$$

$$P = U \cdot I \cdot \cos \varphi$$

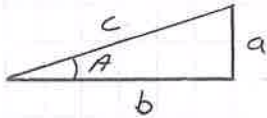

$$\sin A = \frac{a}{c}$$

$$\cos A = \frac{b}{c}$$

$$\tan A = \frac{a}{b}$$

$$c^2 = a^2 + b^2$$

Virsvæðleiki á forvati:


$$A = \frac{I}{J}$$

A = þverflatarmál
J = 2,8 = straum
þéttleiki

Spennar:

Stráumur
á forvati:

$$I = \frac{S}{U}$$

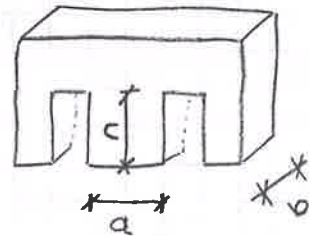

All sem hægt er að yfirtæna

$$S = \text{sýndaröfl}$$

$$VK = a \cdot b \cdot c$$


$$dW = \frac{a}{2}$$

$$S = \frac{VK \cdot dW}{0,8}$$

$$\epsilon = \epsilon_0 \cdot \epsilon_r$$

ϵ_0 = ratsvari loftlæmis

ϵ_r = ratsvari efnis

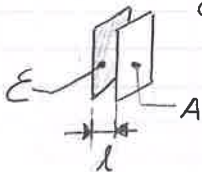

l = fjarlægð milli plötanna

A = Flatarmál plötanna

$$C = \frac{\epsilon_r \cdot \epsilon_0 \cdot A}{l}$$

Taplaus spennir:

$$\frac{U_1}{U_2} = \frac{N_1}{N_2} = \frac{I_2}{I_1}$$