



Method: $U_{CE} = 0V$

$$I_C(\text{SAT}) = \frac{U}{R_C} = \frac{12V}{300\Omega} = 40\text{ mA}$$

Rot: Punktur (U_{CE}, I_C)

$I_C = 0 \Rightarrow U_{CE} = U$

Punktur (U_{CE}, I_C)

