

# Sýnidæmi einfasa spennir

$$S = 5 \text{ kVA}$$

$$U_1 = 230 \text{ V}$$

$$U_2 = 12 \text{ V}$$

$$\eta = 0,85$$

1) Reikna breytihlutfall  $u$

$$u = \frac{U_1}{U_2} = \frac{230 \text{ V}}{12 \text{ V}} = \underline{\underline{19,17}}$$

2) Reikna  $N_1$  ef  $N_2 = 200$

$$u = \frac{N_1}{N_2} \Rightarrow N_1 = u \cdot N_2 = 19,17 \cdot 200 = \underline{\underline{3834 \text{ vindingar}}}$$


3) Reikna málstrámm á eftirvati

$$I_2 = \frac{S_2}{U_2} = \frac{5 \cdot 10^3 \text{ VA}}{12 \text{ V}} = \underline{\underline{416,7 \text{ A}}}$$

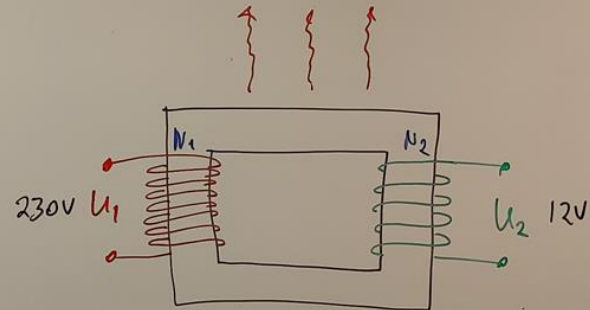4) Reikna málstrámm á forvati

$$S_1 = \frac{S_2}{\eta} = \frac{5 \cdot 10^3 \text{ VA}}{0,85} = 5882 \text{ VA}$$

$$I_1 = \frac{S_1}{U_1} = \frac{5882 \text{ VA}}{230 \text{ V}} = 25,6 \text{ A}$$



$$\eta = \frac{P_2}{P_1}$$

$$u = \frac{U_1}{U_2} = \frac{N_1}{N_2}$$

$$\text{Ef } \cos \varphi = 1$$

$$\text{þá er } \eta = \frac{S_2}{S_1}$$